

# **TS3003 Demo Board**

# A 1.55V to 5.25V, 1.9µA, 9kHz to 300kHz Silicon Timer

### **FEATURES**

- ➣ 5V Supply Voltage
- FOUT/PWMOUT Output Period: 40μs(25kHz)
   RSET = 4.32MΩ
  - > PWMOUT Output Duty Cycle:
  - 75% with CPWM = 100pF
- > PWMOUT Duty Cycle Reduction
  - 1MΩ Potentiometer
- Fully Assembled and Tested
- > 2in x 2in 2-layer circuit board

# **COMPONENT LIST**

DESIGNATION	QTY	DESCRIPTION
C1	1	100pF ±10%
		capacitor (0805)
C2	1	4.7µF ±10%
		capacitor (0805)
R2	1	10MΩ ± 1% (0805)
R1	1	$4.32M\Omega \pm 1\% (0805)$
PWM_ADJ	1	1MΩ Potentiometer
U1	1	TS3003
VDD,F_OUT,	3	Test points
PWM_OUT		·
J1	1	Jumper

# Touchstone SEMICONDUCTOR (408)-383-9363 TS3003 DEMO BOARD PI C1 PWM\_OUT VDD GND C2 R1 F\_OUT

Figure 1. TS3003 Demo Board (Top View)

# **DESCRIPTION**

The TS3003 is a single-supply, second-generation oscillator/timer fully specified to operate at a supply voltage range of 1.55V to 5.25V while consuming less than 2.4μA(max) supply current. Requiring only a resistor to set the base output frequency (or output period) at 25kHz (or 40μs) with a 50% duty cycle, the TS3003 timer/oscillator is compact, easy-to-use, and versatile. Optimized for ultra-long life, low frequency, battery-powered/portable applications, the TS3003 joins the TS3001, TS3002, TS3004, and TS3006 in the timer family of the "NanoWatt Analog<sup>TM</sup>" series of high-performance analog integrated circuits.

The TS3003 requires only an RSET =  $4.32M\Omega$  resistor to set the FOUT/PWMOUT output period to  $40\mu s(25kHz)$ . With an on-board 100pF CPWM capacitor, the duty cycle of PWMOUT is set at approximately 75%. Further reduction of the duty cycle is available with an on-board  $1M\Omega$  potentiometer. The complete circuit is designed at a supply voltage of 5V. The TS3003 is fully specified over the -40°C to +85°C temperature range and is available in a low-profile, 10-pin 3x3mm TDFN package with an exposed back-side paddle.

Product data sheet and additional documentation can be found at <a href="https://www.silabs.com">www.silabs.com</a>.

# ORDERING INFORMATION

Order Number	Description
TS3003DB	TS3003
	Demo Board



Figure 2. TS3003 Demo Board (Bottom View)

# **TS3003 Demo Board**



## DESCRIPTION

The TS3003 requires only an RSET =  $4.32M\Omega$  resistor to set the FOUT/PWMOUT output period to  $40\mu s(25kHz)$ . With an on-board 100pF CPWM capacitor, the duty cycle of PWMOUT is set at approximately 75%. Further reduction of the duty cycle is available with an on-board  $1M\Omega$  potentiometer. The complete circuit is designed at a supply voltage of 5V and it is shown in Figure 1.

The TS3003 is a user-programmable oscillator where the period of the square wave at its FOUT terminal is generated by an external resistor connected to the RSET pin. The output period is given by:

$$FOUT (Hz) = \frac{1.08E11}{RSET}$$

**Equation 1.** FOUT Frequency Calculation

With  $R_{SET} = 4.32 M\Omega$ , the FOUT period is approximately 40µs (25kHz) with a 50% duty cycle. As design aids, Tables 1 lists TS3003's typical FOUT frequency for various standard values for  $R_{SET}$ .

R <sub>SET</sub> (MΩ)	FOUT (kHz)
0.360	300
1	108
2.49	43.37
4.32	25
6.81	15.86
9.76	11.07
12	9

Table 1: FOUT vs RSET

The TS3003 also provides a separate PWM output signal at its PWMOUT terminal that is anti-phase with respect to FOUT. To adjust the pulse width of the PWMOUT output, a single capacitor can be placed at the CPWM pin. To determine the capacitance needed for a desired pulse width, the following equation is to be used:

$$CPWM(F) = \frac{Pulse \ Width(s) \ x \ I_{CPWM}}{V_{CPWM} \cong 300mV}$$

**Equation 2.** CPWM Capacitor Calculation

where  $I_{\text{CPWM}}$  and  $V_{\text{CPWM}}$  is the current supplied and voltage applied to the CPWM capacitor, respectively.

The pulse width is determined based on the period of FOUT and should never be greater than the period at FOUT. Make sure the PWM\_CNTRL pin is set to at least 400mV when calculating the pulse width of PWMOUT. Note  $V_{\text{CPWM}}$  is approximately 300mV, which is the RSET voltage. Also note that  $I_{\text{CPWM}}$  is approximately 1 $\mu$ A.

# **QUICK START PROCEDURE**Required Equipment

- > TS3003 Demo Board
- DC Power Supply
- Oscilloscope Model Agilent DSO1014A or equivalent
- Two 10X, 15pF//10MΩ oscilloscope probes
- Potentiometer screwdriver

To evaluate the TS3003 silicon timer, the following steps are to be performed:

- Before connecting the DC power supply to the demo board, turn on the power supply, set the DC voltage to 5V, and then turn it off.
- Connect the DC power supply positive terminal to the test point labeled VDD. Connect the negative terminal of the DC power supply to the test point labeled GND.
- To monitor the FOUT output signal, connect the signal terminal of an oscilloscope probe to the test point labeled FOUT and the ground terminal to the test point labeled GND.
- 4) To monitor the PWMOUT output signal, connect the signal terminal of a second oscilloscope probe to the test point labeled PWM\_OUT and the ground terminal to the test point labeled GND.
- 5) Select two channels on the oscilloscope and set the vertical voltage scale and the vertical position on each channel to 2V/DIV and 0V, respectively. Set the horizontal time scale to 5μs/DIV. The coupling should be DC coupling. Turn on the power supply.

The supply current will vary depending on the load on the output. Given the default set-up on the board, the FOUT/PWMOUT output period is approximately 40µs. The PWMOUT duty cycle is set to approximately 75%. With an output load of

TS3003-EVB Rev. 1.0 Page 2



# **TS3003 Demo Board**

15pF on both FOUT and PWMOUT outputs due to the oscilloscope probes, the supply current should be less than  $8\mu A$ .

6) If further reduction of the duty cycle of the PWMOUT output is desired, turn the potentiometer clockwise. If jumper J1 is removed, the PWM\_CNTRL pin is tied to VDD and the potentiometer will not change the PWMOUT output duty cycle.

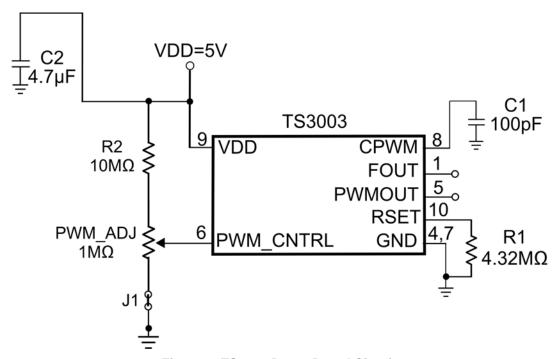


Figure 3. TS3003 Demo Board Circuit

TS3003-EVB Rev. 1.0 Page 3



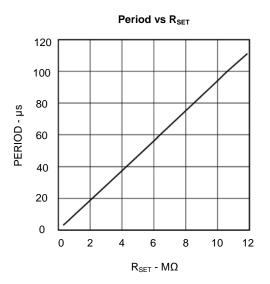


Figure 4. FOUT/PWMOUT Period vs RSET

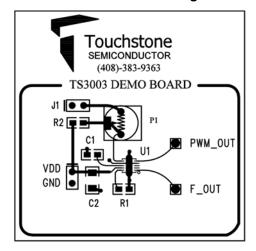


Figure 5. Top Layer View #1

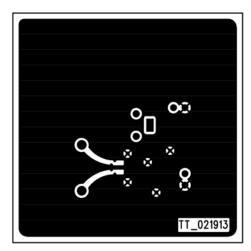


Figure 7. Bottom Layer (GND) #1


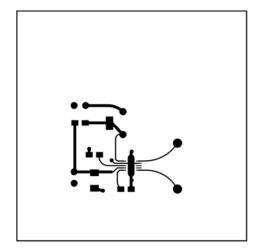


Figure 6. Top Layer View #2

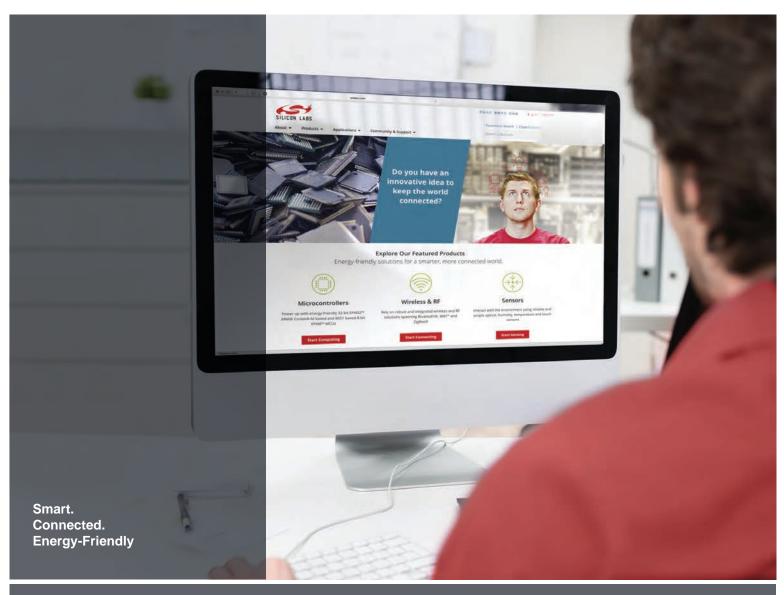

Figure 8. Bottom Layer (GND) #2









### Disclaimer

Silicon Laboratories intends to provide customers with the latest, accurate, and in-depth documentation of all peripherals and modules available for system and software implementers using or intending to use the Silicon Laboratories products. Characterization data, available modules and peripherals, memory sizes and memory addresses refer to each specific device, and "Typical" parameters provided can and do vary in different applications. Application examples described herein are for illustrative purposes only. Silicon Laboratories reserves the right to make changes without further notice and limitation to product information, specifications, and descriptions herein, and does not give warranties as to the accuracy or completeness of the included information. Silicon Laboratories shall have no liability for the consequences of use of the information supplied herein. This document does not imply or express copyright licenses granted hereunder to design or fabricate any integrated circuits. The products must not be used within any Life Support System without the specific written consent of Silicon Laboratories. A "Life Support System" is any product or system intended to support or sustain life and/or health, which, if it fails, can be reasonably expected to result in significant personal injury or death. Silicon Laboratories products are generally not intended for military applications. Silicon Laboratories products shall under no circumstances be used in weapons of mass destruction including (but not limited to) nuclear, biological or chemical weapons, or missiles capable of delivering such weapons.

### **Trademark Information**

Silicon Laboratories Inc., Silicon Laboratories, Silicon Labs, SiLabs and the Silicon Labs logo, CMEMS®, EFM, EFM32, EFR, Energy Micro, Energy Micro logo and combinations thereof, "the world's most energy friendly microcontrollers", Ember®, EZLink®, EZMac®, EZRadio®, EZRadioPRO®, DSPLL®, ISOmodem ®, Precision32®, ProSLIC®, SiPHY®, USBXpress® and others are trademarks or registered trademarks of Silicon Laboratories Inc. ARM, CORTEX, Cortex-M3 and THUMB are trademarks or registered trademarks of ARM Holdings. Keil is a registered trademark of ARM Limited. All other products or brand names mentioned herein are trademarks of their respective holders.



Silicon Laboratories Inc. 400 West Cesar Chavez Austin, TX 78701